

**Department of Electronic and Telecommunication
Engineering**

University of Moratuwa

EN2111 Electronic Circuit Design



UART Implementation on FPGA

Cooray P.L.L.K. - 210088L

Dabare A.D.T. - 210089P

Dassanayake D.M.T.K. - 210095F

Group No. : **12**

Date : 05/08/2024

Content

1. Introduction	3
2. Verilog HDL Code	3
2.1 Transmitter	3
2.2 Receiver	4
2.3 Baud rate	5
2.4 Top-Level Entity	6
2.5 Test Bench	7
3. Simulation Results	8

1. Introduction

UART, a popular serial communication protocol, enables devices to exchange data efficiently. Unlike bulky parallel connections, UART transmits data one bit at a time over a single wire. This simplicity comes at a cost - there's no constant clock signal for synchronization. To overcome this, UART utilizes start and stop bits to mark the beginning and end of data packets, ensuring the receiving device interprets information correctly. Additionally, both devices must agree on a specific transmission speed (baud rate) for error-free communication. Implementing UART on a DE0-Nano FPGA board involves creating a Verilog program that defines the data conversion process and incorporates start/stop bits. This program is then tested and uploaded to the board. Finally, the board's designated pins (Tx for transmit and Rx for receive) are connected to the other device, allowing them to seamlessly exchange data.

2. Verilog HDL Code

2.1 Transmitter

```
1  module transmitter( input wire [7:0] data_in, //input data as an 8-bit register/vector
2                     input wire wr_en, //enable wire to start
3                     input wire clk_50m,
4                     input wire clken, //clock signal for the transmitter
5                     output reg Tx, //a single 1-bit register variable to hold transmitting bit
6                     output wire Tx_busy //transmitter is busy signal
7                     );
8
9  initial begin
10     Tx = 1'b1; //initialize Tx = 1 to begin the transmission
11 end
12 //Define the 4 states using 00,01,10,11 signals
13 parameter TX_STATE_IDLE = 2'b00;
14 parameter TX_STATE_START = 2'b01;
15 parameter TX_STATE_DATA = 2'b10;
16 parameter TX_STATE_STOP = 2'b11;
17
18 reg [7:0] data = 8'h00; //set an 8-bit register/vector as data, initially equal to 00000000
19 reg [2:0] bit_pos = 3'h0; //bit position is a 3-bit register/vector, initially equal to 000
20 reg [1:0] state = TX_STATE_IDLE; //state is a 2 bit register/vector, initially equal to 00
21
22 always @(posedge clk_50m) begin
23     case (state) //Let us consider the 4 states of the transmitter
24         TX_STATE_IDLE: begin //We define the conditions for idle or NOT-BUSY state
25             if (~wr_en) begin
26                 state <= TX_STATE_START; //assign the start signal to state
27                 data <= data_in; //we assign input data vector to the current data
28                 bit_pos <= 3'h0; //we assign the bit position to zero
29             end
30         end
31         TX_STATE_START: begin //We define the conditions for the transmission start state
32             if (clken) begin
33                 Tx <= 1'b0; //set Tx = 0 indicating transmission has started
34                 state <= TX_STATE_DATA;
35             end
36         end
37         TX_STATE_DATA: begin
38             if (clken) begin
39                 if (bit_pos == 3'h7) //we keep assigning Tx with the data until all bits have been transmitted from 0 to 7
40                     state <= TX_STATE_STOP; // when bit position has finally reached 7, assign state to stop transmission
41                 else
42                     bit_pos <= bit_pos + 3'h1; //increment the bit position by 001
43                 Tx <= data[bit_pos]; //Set Tx to the data value of the bit position ranging from 0-7
44             end
45         end
46         TX_STATE_STOP: begin
47             if (clken) begin
48                 Tx <= 1'b1; //set Tx = 1 after transmission has ended
49                 state <= TX_STATE_IDLE; //Move to IDLE state once a transmission has been completed
50             end
51         end
52         default: begin
53             Tx <= 1'b1; // always begin with Tx = 1 and state assigned to IDLE
54             state <= TX_STATE_IDLE;
55         end
56     end
57 end
```

```

56     endcase
57 end
58
59 assign Tx_busy = (state != TX_STATE_IDLE); //We assign the BUSY signal when the transmitter is not idle
60
61 endmodule
62

```

2.2 Receiver

```

1  module receiver (input wire Rx,
2                    output reg ready, // default 1 bit reg
3                    input wire ready_clr,
4                    input wire clk_50m,
5                    input wire clken,
6                    output reg [7:0] data // 8 bit register
7                );
8  initial begin
9      ready = 1'b0; // initialize ready = 0
10     data = 8'b0; // initialize data as 00000000
11 end
12 // Define the 4 states using 00,01,10 signals
13 parameter RX_STATE_START = 2'b00;
14 parameter RX_STATE_DATA = 2'b01;
15 parameter RX_STATE_STOP = 2'b10;
16
17 reg [1:0] state = RX_STATE_START; // state is a 2-bit register/vector, initially equal to 00
18 reg [3:0] sample = 0; // This is a 4-bit register
19 reg [3:0] bit_pos = 0; // bit position is a 4-bit register/vector, initially equal to 000
20 reg [7:0] scratch = 8'b0; // An 8-bit register assigned to 00000000
21
22 always @(posedge clk_50m) begin
23     if (ready_clr)
24         ready <= 1'b0; // This resets ready to 0
25
26     if (clken) begin
27         case (state) // Let us consider the 3 states of the receiver
28             RX_STATE_START: begin // We define conditions for starting the receiver
29                 if (IRx || sample != 0) // start counting from the first low sample
30                     sample <= sample + 4'b1; // increment by 0001
31                 if (sample == 15) begin // once a full bit has been sampled
32                     state <= RX_STATE_DATA; // start collecting data bits
33                     bit_pos <= 0;
34                     sample <= 0;
35                     scratch <= 0;
36                 end
37             end
38             RX_STATE_DATA: begin // We define conditions for starting the data collecting
39                 sample <= sample + 4'b1; // increment by 0001
40                 if (sample == 4'h8) begin // we keep assigning Rx data until all bits have 01 to 7
41                     scratch[bit_pos[2:0]] <= Rx;
42                     bit_pos <= bit_pos + 4'b1; // increment by 0001
43                 end
44                 if (bit_pos == 8 && sample == 15) // when a full bit has been sampled and
45                     state <= RX_STATE_STOP; // bit position has finally reached 7, assign state to
46         stop
47     end

```

```

47     RX_STATE_STOP: begin
48         /*
49          * Our baud clock may not be running at exactly the
50          * same rate as the transmitter. If we think that
51          * we're at least half way into the stop bit, allow
52          * transition into handling the next start bit.
53          */
54         if (sample == 15 || (sample >= 8 && !Rx)) begin
55             state <= RX_STATE_START;
56             data <= scratch;
57             ready <= 1'b1;
58             sample <= 0;
59         end
60     else begin
61         sample <= sample + 4'b1;
62     end
63 end
64 default: begin
65     state <= RX_STATE_START; // always begin with state assigned to START
66 end
67 endcase
68 end
69 end
70
71 endmodule
72

```

2.3 Baud Rate

```

1  //This is a baud rate generator to divide a 50MHz clock into a 115200 baud Tx/Rx pair.
2  //The Rx clock oversamples by 16x.
3
4  module baudrate (input wire clk_50m,
5                   output wire Rxcclk_en,
6                   output wire Txcclk_en
7                   );
8
9  //Our Testbench uses a 50 MHz clock.
10 //Want to interface to 115200 baud UART for Tx/Rx pair
11 //Hence, 50000000 / 115200 = 435 clocks Per Bit.
12 parameter RX_ACC_MAX = 50000000 / (115200 * 16);
13 parameter TX_ACC_MAX = 50000000 / 115200;
14 parameter RX_ACC_WIDTH = $clog2(RX_ACC_MAX);
15 parameter TX_ACC_WIDTH = $clog2(TX_ACC_MAX);
16 reg [RX_ACC_WIDTH - 1:0] rx_acc = 0;
17 reg [TX_ACC_WIDTH - 1:0] tx_acc = 0;
18
19 assign Rxcclk_en = (rx_acc == 5'd0);
20 assign Txcclk_en = (tx_acc == 9'd0);
21
22 always @(posedge clk_50m) begin
23     if (rx_acc == RX_ACC_MAX[RX_ACC_WIDTH - 1:0])
24         rx_acc <= 0;
25     else
26         rx_acc <= rx_acc + 5'b1; //increment by 00001
27 end
28
29 always @(posedge clk_50m) begin
30     if (tx_acc == TX_ACC_MAX[TX_ACC_WIDTH - 1:0])
31         tx_acc <= 0;
32     else
33         tx_acc <= tx_acc + 9'b1; //increment by 000000001
34 end
35
36 endmodule
37

```

2.4 Top - Level Entity

```
1  module uart(input wire [7:0] data_in, //input data
2              input wire wr_en,
3              input wire clear,
4              input wire clk_50m,
5              output wire Tx,
6              output wire Tx_busy,
7              input wire Rx,
8              output wire ready,
9              input wire ready_clr,
10             output wire [7:0] data_out,
11             output [7:0] LEDR,
12             output wire Tx2//output data
13             );
14  assign LEDR = data_in;
15  assign Tx2 = Tx;
16  wire Txclk_en, Rxclk_en;
17  baudrate uart_baud( .clk_50m(clk_50m),
18                    .Rxclk_en(Rxclk_en),
19                    .Txclk_en(Txclk_en)
20                    );
21  transmitter uart_Tx( .data_in(data_in),
22                    .wr_en(wr_en),
23                    .clk_50m(clk_50m),
24                    .clken(Txclk_en), //we assign Tx clock to enable clock
25                    .Tx(Tx),
26                    .Tx_busy(Tx_busy)
27                    );
28  receiver uart_Rx( .Rx(Rx),
29                    .ready(ready),
30                    .ready_clr(ready_clr),
31                    .clk_50m(clk_50m),
32                    .clken(Rxclk_en), //we assign Tx clock to enable clock
33                    .data(data_out)
34                    );
35
36  endmodule
37
```

2.5 Test Bench


Date: May 08, 2024

uart_TB.v


Project: uart_tx_rx

```
1  module uart_TB();
2
3  reg [7:0] data = 0;           // Initialize data to 0
4  reg clk = 0;
5  reg enable = 0;
6
7  wire Tx_busy;
8  wire ready;
9  wire [7:0] Rx_data;
10
11 wire loopback;
12 reg ready_clr = 0;
13
14 // Instantiation of uart module
15 uart test_uart(.data_in(data),
16                .wr_en(enable),
17                .clk_50m(clk),
18                .Tx(loopback),
19                .Tx_busy(Tx_busy),
20                .Rx(loopback),
21                .ready(ready),
22                .ready_clr(ready_clr),
23                .data_out(Rx_data)
24                );
25 initial begin
26     $dumpfile("uart.vcd");
27     $dumpvars(0, uart_TB);
28     enable <= 1'b1;
29     #2 enable <= 1'b0;
30 end
31
32
33 // Behavior upon reception of ready signal from UART module
34 always @(posedge ready) begin
35     #2 ready_clr <= 1;
36     #2 ready_clr <= 0;
37     if (Rx_data != data)           // Check if received data matches transmitted data
38     begin
39         $display("FAIL: rx data %x does not match tx %x", Rx_data, data);
40         $finish;
41     end
42     else begin
43         if (Rx_data == 8'h2) begin // Check if received data is 11111111
44             $display("SUCCESS: all bytes verified");
45             $finish;
46         end
47
48         enable <= 1'b1;           // Enable UART module
49         data <= data + 1'b1;       // Increment transmitted data
50         #2 enable <= 1'b0;         // Disable UART module after 2 time units
51     end
52 end
53 // Clock generation
54 always begin
55     #1 clk = ~clk;
56 end
57 endmodule
58
```

Testbench results

 


Transmitted bits

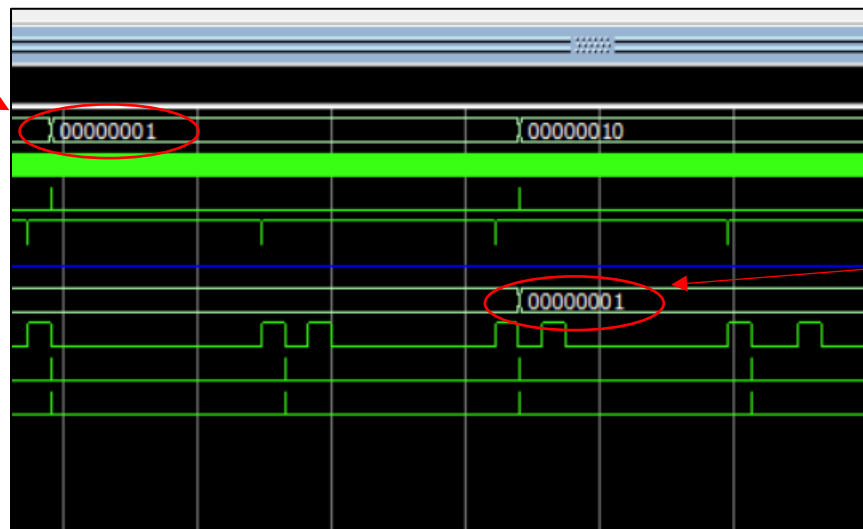


- Received bits

RTL Viewer

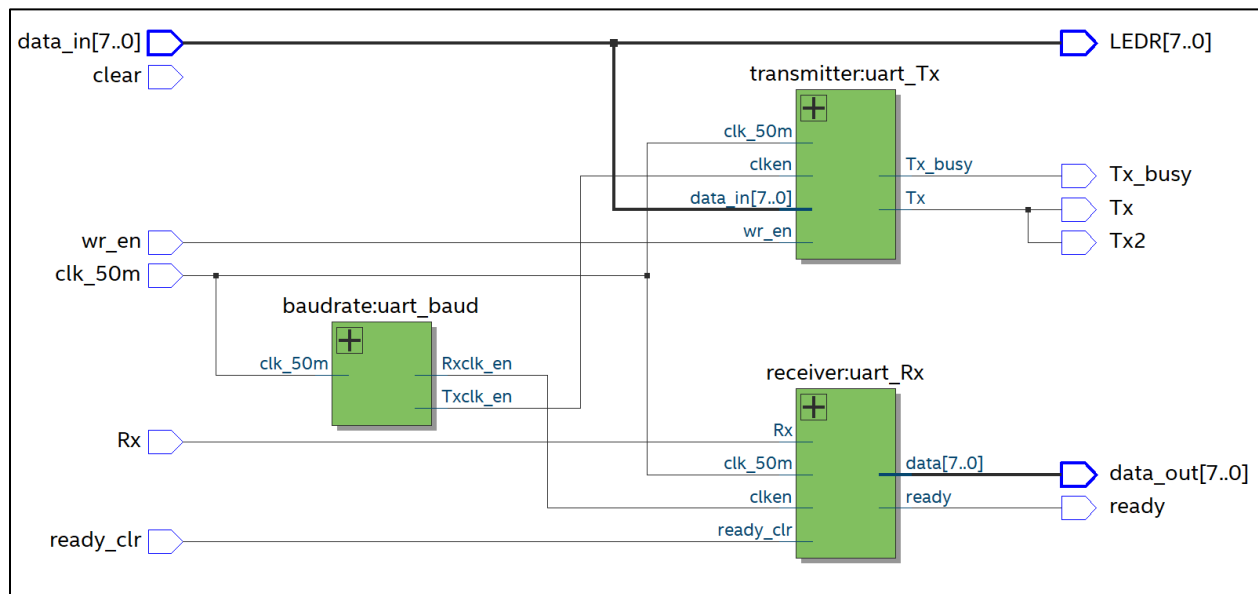

FPGA Implementation

 

References

[1] M. Maged, “MuhammadMajiid/UART,” *GitHub*, Apr. 17, 2024.
<https://github.com/MuhammadMajiid/UART> (accessed May 08, 2024).

[2] “UART & FPGA Bluetooth connection | Road to FPGAs #104,” [www.youtube.com](https://www.youtube.com/watch?v=QlscDcbKUV4).
<https://youtu.be/QlscDcbKUV4?si=bgv5kwBHtRHo2gAz> (accessed May 08, 2024).